



Asynchronous Design Seminar at University of Verona – Lecture Notes 2

Asynchronous Design Fundamentals



Bundled-Data Pipelines

Micropipelines and Mousetrap




2

Asynchronous Control Circuit Design - L2 5/28/2016

The C Element

► AND gate for events

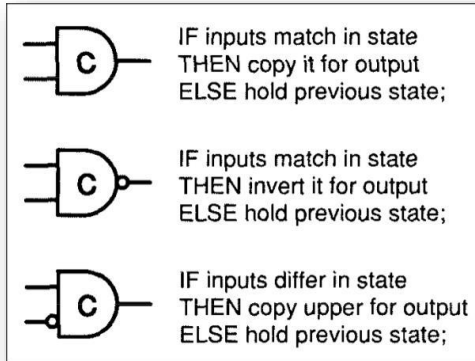


a	b	c
0	0	0
0	1	c'
1	0	c'
1	1	1

► What is the OR gate equivalent for events?


► 3

Asynchronous Control Circuit Design - L2 5/28/2016

C-Element Implementations

 

Dynamic C-Element

 

Static C-Element

► 4

Asynchronous Control Circuit Design - L2 5/28/2016

C-Element Implementations

► Using Standard Cells



► 2-input C-Element's Logic Function is:

$$c = ab + c(a + b) = ab + bc + ac$$

► n-input C-Element is:

$$c = a_1 a_2 \dots a_n + c(a_1 + a_2 + \dots + a_n)$$

  ► Thus may be implemented using two level logic or using an SR latch




► 5


Asynchronous Control Circuit Design - L2 5/28/2016

C Gate Formal Models

FSM

 


PTnet

 

► 6

Asynchronous Control Circuit Design - L2 5/28/2016

Micropipeline Control Structure

 


- ▶ Req/Ack are handshaking pairs
- ▶ $C[i]$ accepts I/O from $C[i-1]$ only if $C[i+1]=0/1$
- ▶ Think of 1010101.. as waves: 1₀ 1₀ 1₀ 1..
- ▶ The C-elements propagate waves precisely
- ▶ Timing depends on local delays, may vary along the pipe
- ▶ If RIGHT is quiet, pipe will fill and stall
- ▶ Same for 4-phase, 2-phase

▶ 7

Asynchronous Control Circuit Design - L2 5/28/2016

Micropipeline Analysis - PTnets

- ▶ Two-stage Micropipeline PTnet:

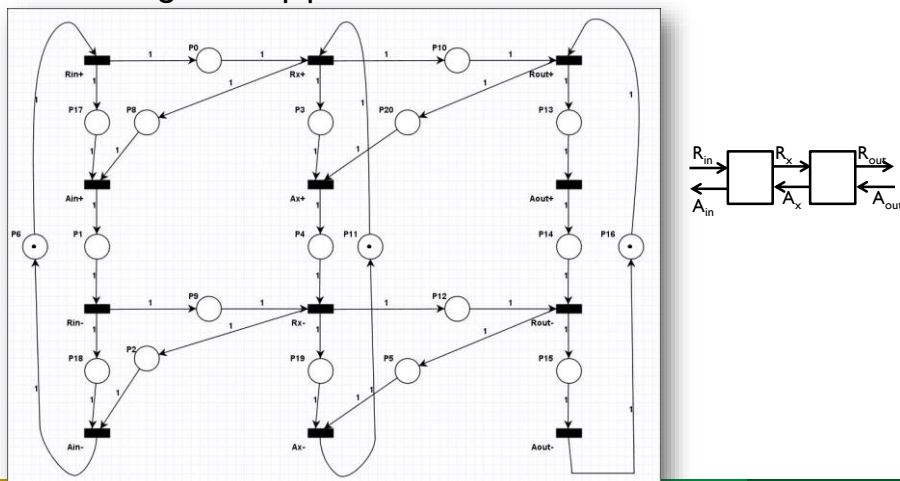


▶ 8

Asynchronous Control Circuit Design - L2 5/28/2016

Micropipeline Analysis - PTnets

► Four-stage Micropipeline PTnet:

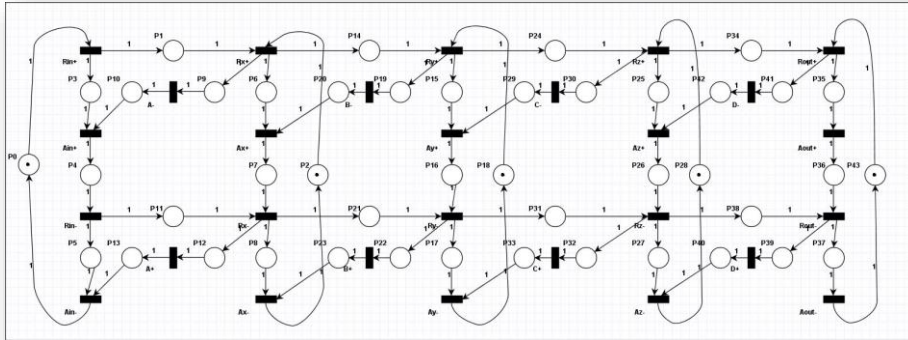

- Represents 4 C Elements and their environments
- **Correct operation may be verified by possible signal orders**


► 9

Asynchronous Control Circuit Design - L2 5/28/2016

Micropipeline Analysis - PTnets

► Four-stage Micropipeline Ptnet

► Reduction to Latch Control Signals

 

► Characteristic Pattern:




► 10

Asynchronous Control Circuit Design - L2 5/28/2016


Micropipeline Analysis - MSFSMs

Two-stage Micropipeline FSMs:

First stage FSM

 

Second stage FSM

 


What about LHS/RHS FSM Interfaces?

What are the two environment FSMs $Rin/Ain, Rout/Aout$?

► 11

Asynchronous Control Circuit Design - L2 5/28/2016

Bundled-Data Concept

 


- Static combinational logic (typically) and standard FFs or latches
- Channels use bundled-data protocol
 - Data lines of the channel are "bundled" timing-wise to the REQ line, so:
 - $time(valid, REQ) > time(valid, data)$
 - Delay line matches worst-case delay of combinational logic
 - Margin limits performance, particularly because adds to forward latency
- Controller CTRL drives local clock to bank of FFs (or latches)
 - Designed using known templates or burst-mode controllers, signal-transition graphs, or syntax directed translation

► 12

Asynchronous Control Circuit Design - L2 5/28/2016

Four-Phase Micropipeline

 


- ▶ Latches are active high
- ▶ Four-phase, so latches open on first $\frac{1}{2}$ of h/s and close on second $\frac{1}{2}$

▶ 13

Asynchronous Control Circuit Design - L2 5/28/2016

Four-Phase Micropipeline Stage

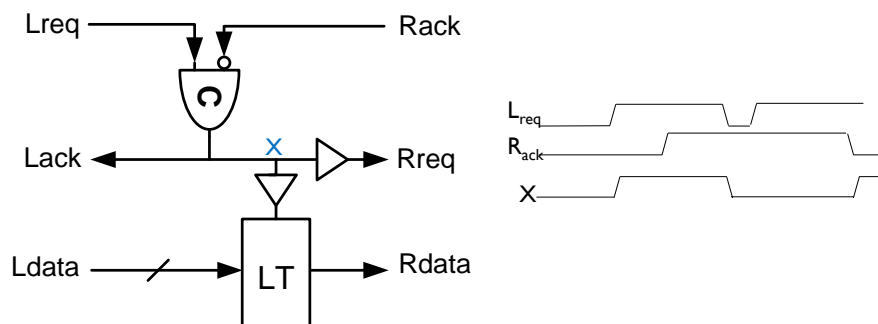


Note: Latch is level-sensitive

- ▶ Four-phase protocol on L_{req}/L_{ack} and R_{req}/R_{ack}
 - ▶ Latch is simple level sensitive traditional latch
 - ▶ This is a Half-Buffer!

▶ 14

Asynchronous Control Circuit Design - L2 5/28/2016

Four-Phase Micropipeline with C.L.

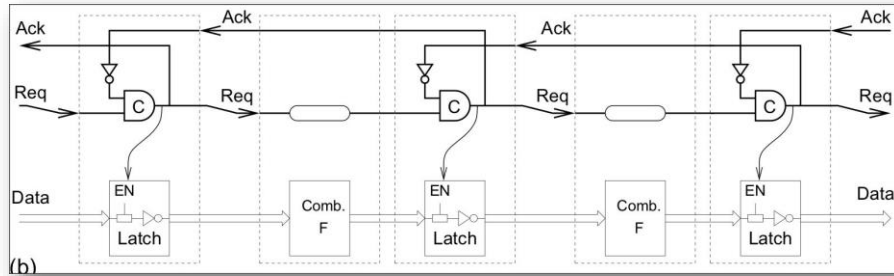


- ▶ Delay elements **mimic** worst-case critical path of Combinational Logic Cloud, F, of each pipe stage
- ▶ Bundled-Data Design (bundling assumption on Req, Data)

▶ 15

Asynchronous Control Circuit Design - L2 5/28/2016

Micropipeline 4-Phase PTnet including Latch Enable

 
- ▶ L
 - ▶ **Active-high** in PTnet
- ▶ L^-
 - ▶ Closes Latch
- ▶ L^+
 - ▶ Opens Latch




▶ 16

Asynchronous Control Circuit Design - L2 5/28/2016

Two Phase Signaling

 

 
- ▶ Every Toggle on request => new data
- ▶ Seems to be faster (NRZ)
 - ▶ Not in general
- ▶ Seems to be low power
 - ▶ Not usually the case
- ▶ More complex Control
 - ▶ Data Validity coded in phase difference of Req & Ack



▶ 17

Asynchronous Control Circuit Design - L2 5/28/2016

Two-Phase Micropipeline


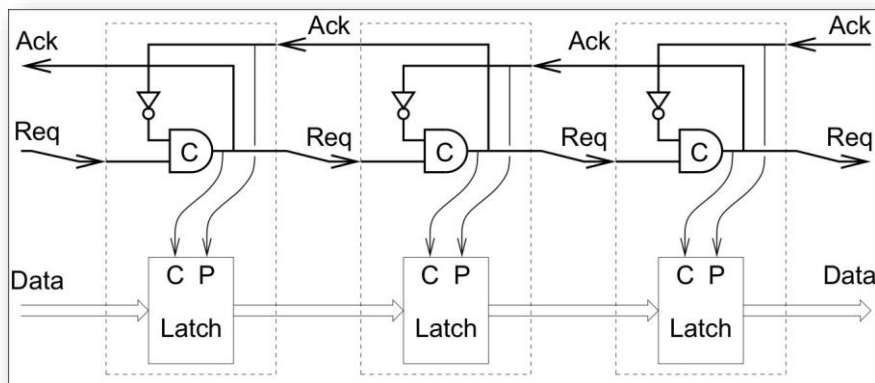


- ▶ Simple version without Cd (C done), Pd (P done)
 - ▶ Little difference anyway in generating fake done signals (using delay elements)

▶ 18

Asynchronous Control Circuit Design - L2 5/28/2016

Capture-Pass Data Latch

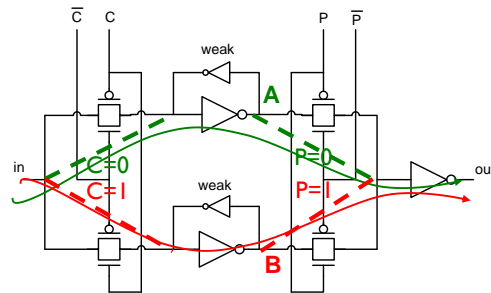 

Two-phase data-latch

- ▶ Becomes transparent when a Pass "P" event occurs
- ▶ Becomes opaque when a Capture "C" event occurs
- ▶ Store data alternatively in top and bottom inverter loops

▶ $(C == P) \rightarrow \text{open}$

▶ $(C \neq P) \rightarrow \text{closed}$


▶ Transition signalling

Too many Transistors

▶ 19

Asynchronous Control Circuit Design - L2 5/28/2016

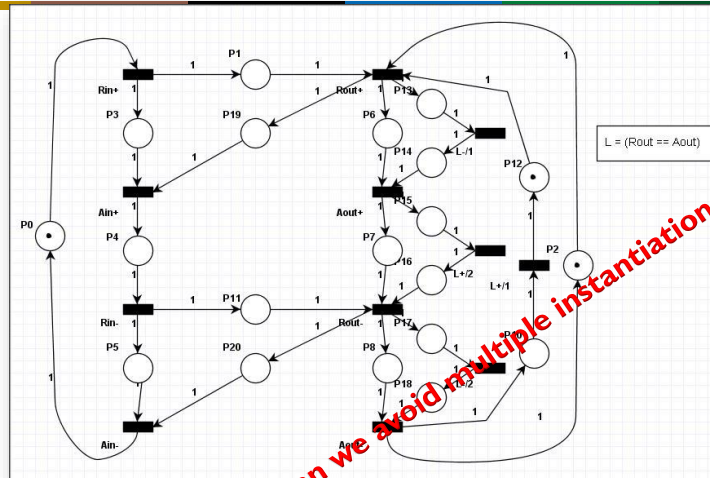Micropipeline 2-Phase PTnet including Latch Enable




▶ Multiple instantiations of L signal ($L/1, 2$)

▶ 20

Asynchronous Control Circuit Design - L2 5/28/2016

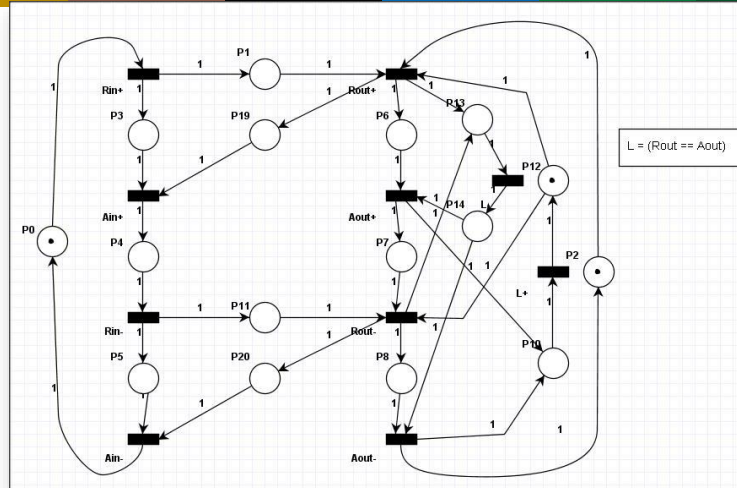Micropipeline 2-Phase PTnet including Latch Enable and Single Latch Signal



► Note the AC Return from Choice/Choice Needed

► 21

Asynchronous Control Circuit Design - L2 5/28/2016

Micropipeline Rings


- So far focused on Linear Pipelines
- A Latch Controller Ring is a very useful structure
 - Data tokens go around the ring
 - Represents basic iterative computation
 - May include entry/exit points
 - How do I build a ring?
 - Connect Rout/Aout of RHS controller to Rin/Ain of a LHS controller
- Does it *always* work with micropipelines?

► 22

Asynchronous Control Circuit Design - L2 5/28/2016

Micropipeline 2-Stage Ring

 - ▶ PTnet Cycles with no tokens → **Deadlock!!!**
- ▶ Commoner's Theorem:
 - ▶ **Deadlocked systems include an unmarked cycle**
- ▶ *Can I find a valid marking to make it live?*




▶ 23

Asynchronous Control Circuit Design - L2 5/28/2016


Micropipeline Analysis - MSFSMs

- ▶ Two-stage Micropipeline FSMs:

First stage FSM

 

Second stage FSM

 


- ▶ **Ring** → $Rin = Rout, Ain = Aout$

- ▶ **Never LIVE!!!**

▶ 24

Asynchronous Control Circuit Design - L2 5/28/2016

Micropipeline 3-Stage Ring

 


► Deadlocked at initial (original) marking

► 25

Asynchronous Control Circuit Design - L2 5/28/2016

Micropipeline Analysis - MSFSMs

► Three-stage Micropipeline Ring FSMs:

 


► Now: $R_{in} = R_{out}$, $A_{in} = A_{out}$

► Live when? R_{out}' , R_y' , R_x initial states

► 26

Asynchronous Control Circuit Design - L2 5/28/2016

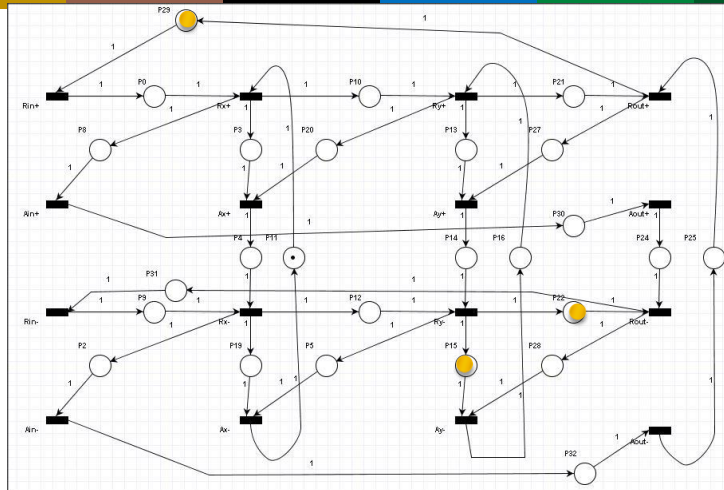Live Micropipeline 3-Stage Ring with Alternate Marking



► Live Marking Shown: Rin^+ , Rx^+ , Ry^-

► 27


Asynchronous Control Circuit Design - L2 5/28/2016

Another interesting example of
FSM-based Formal Analysis

Edge-Triggered FF, Morris Mano Book

►

D-type FF from Mano's Book

 


- ▶ consists of 3 set-reset latches
- ▶ RHS latch produces Q, Q'
- ▶ Verbal functional explanation quite complex and non-intuitive
 - ▶ when **input D is high**, lower LHS latch is set whenever the clock is low
 - ▶ thus, the set input of the upper LHS latch is triggered, which sets the output latch (RHS) whenever the clock is high
 - ▶ when **input is D low**, lower LHS latch is reset, thus resetting the output latch (RHS), whenever the clock is high
- ▶ As a result, Q may only change state when clock makes a low \rightarrow high transition

▶ 29

CE-653 - MSFSM Intuitive Example

D-type FF from Mano's Book

 

- ▶ How can we formally verify that output latch's inputs can never cause race?
 - ▶ are never 00,
OR
 - ▶ can never transition from 00 \rightarrow 11


▶ 30

CE-653 - MSFSM Intuitive Example

Active-Low SR latch

S	R	Q	Q_{next}	\overline{Q}_{next}
0	0	x	1	1
0	1	x	1	0
1	0	x	0	1
1	1	0	0	1
1	1	1	1	0

 - **QUESTION:**
How do we model the sequential SR latch behaviour?




► 31

CE-653 - MSFSM Intuitive Example

Single (Active-Low) SR latch FSM Model

 - Choice between 2 states or 3 states
 - 2 states model hides possibility of $SR = 00$
- $00 \rightarrow 11$ transition result is uncertain, thus the fourth state $QQ' = 11$ does not have deterministic next states
- We assume initial state to be 11
 - May be different, e.g. 01
 - Transitions correspond to SR inputs




► 32

CE-653 - MSFSM Intuitive Example

D-Type FF – inferring MSFSM model

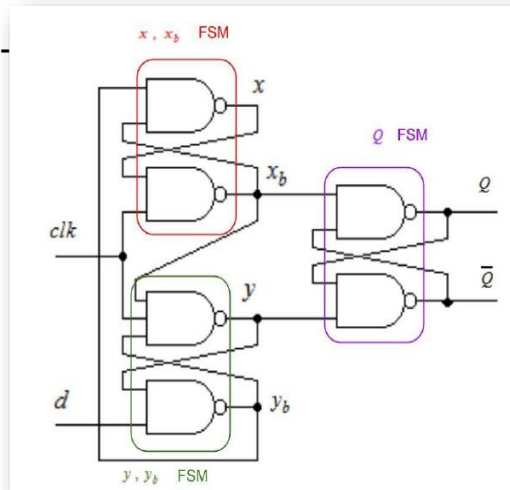
- ▶ We split the D-type FF circuit into 3 separate sub-circuits (SR latches)
- ▶ Infer an FSM of each sub-circuit
- ▶ Signals and states will transition asynchronously
- ▶ Goal:
 - ▶ Signals x_b , y may never assume 00, OR
 - ▶ may never transition from 00 → 11



▶ 33

CE-653 - MSFSM Intuitive Example


FSM #1 - x, x_b signal generation

 


▶ 34

CE-653 - MSFSM Intuitive Example


FSM #2 - y , y_b signal generation

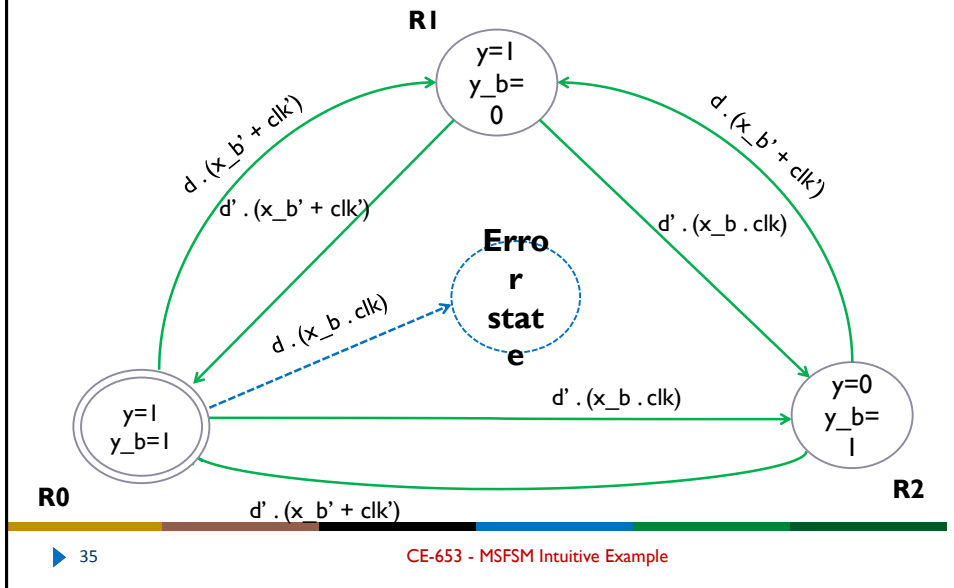

FSM Q - RHS latch output Q

 

Simulating operation using MSFSMs

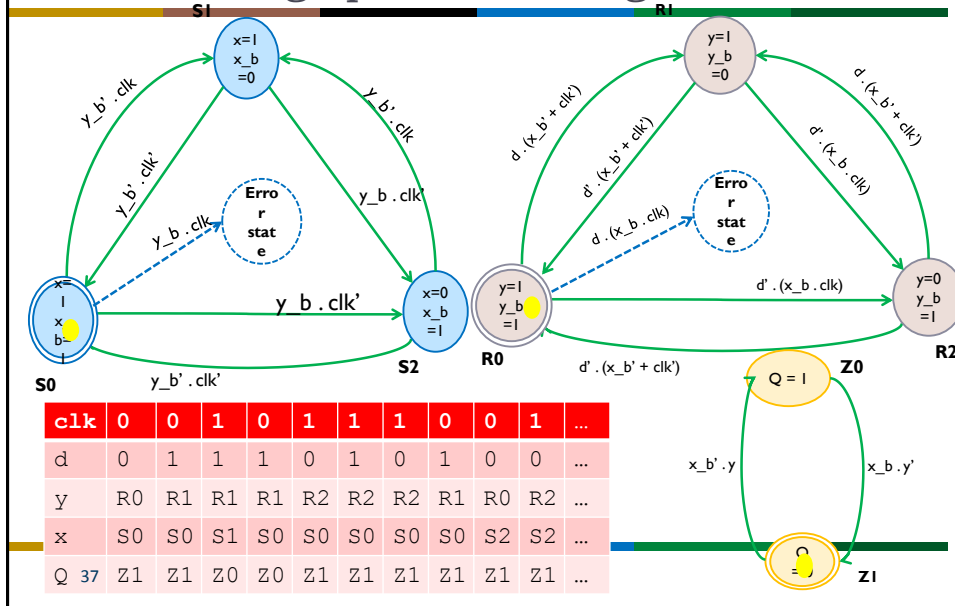


Conclusions

- ▶ The traditional way of verifying a model demands multiplication of FSMs, which leads to bigger state spaces
- ▶ Using interactive FSMs and based on an asynchronous change of signals, we escape the boundaries of a monolithic FSM and avoid state explosion.
- ▶ The state space of the formal analysis in our example was reduced by almost 55%

Mousetrap

 
- ▶ Mousetrap is one of the simplest and fastest latch controller implementations
- ▶ Consists of
 - ▶ XOR gate producing the Latch EN signal
 - ▶ Latch for Storing R_i state
- ▶ Latch is open (transparent) when
 - ▶ $R_0 == A_0$
- ▶ Closes (opaque) when
 - ▶ R_0 changes (1)
- ▶ Opens again when
 - ▶ A_0 changes a second time (1)



▶ 39

Asynchronous Control Circuit Design - L2 5/28/2016

Mousetrap Pipeline

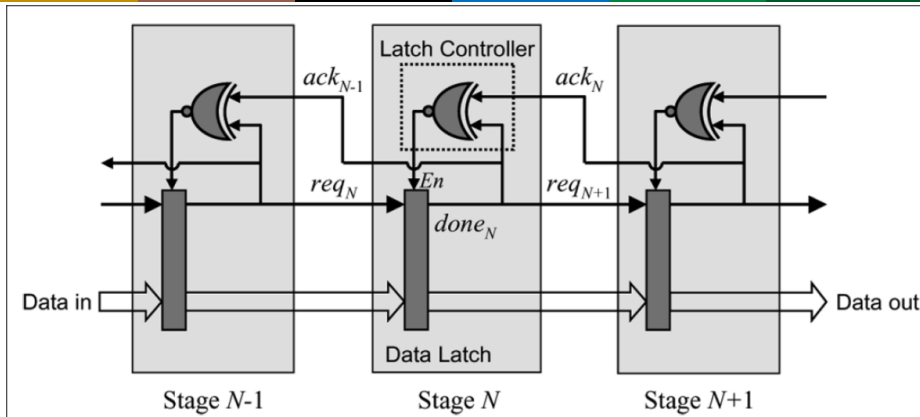


- ▶ Caveat
 - ▶ Does not support feedback dependencies in the Datapath

▶ 40


Asynchronous Control Circuit Design - L2 5/28/2016

Delay Line Design

 


► Symmetric (rise/fall ~same)

 - Designed with an even # of inverters that model worst-case path delay through combinational logic



► Asymmetric (rise slow/fall fast or the opposite)

 - Faster reset implemented by replacing some INVs with NANDs




► Other

- May also use re-create path of gates along critical path to better match delay (delay distribution)

► 41

Asynchronous Control Circuit Design - L2 5/28/2016

Programmable Delay Elements: MUX-DE

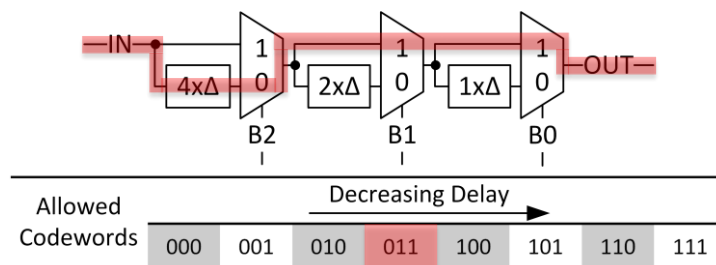


N. Mahapatra et al., "Comparison and Analysis of Delay Elements," in MWSCAS, 2002, pp. 473–476.

- Most popular programmable DE
- Delay controlled by number of buffers in the signal path
- Binary codewords

► 42

Asynchronous Control Circuit Design - L2 5/28/2016

 Speculative Completion Sensing – Variable Latency




- ▶ **Enables data-dependent component delays in bundled-data environment**

▶ 43

Asynchronous Control Circuit Design - L2 5/28/2016

Resilient Bundled Data

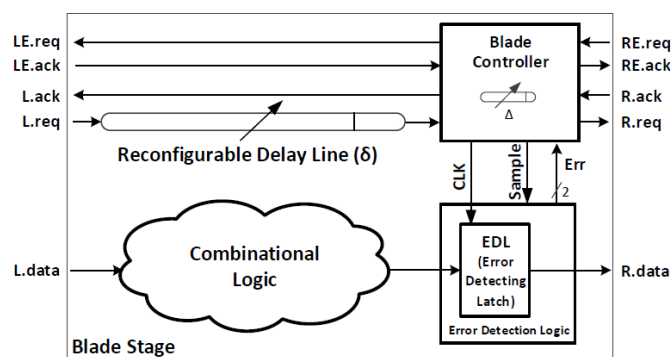

- ▶ Two delay elements
- ▶ Average case performance


D. Hand, M. Moreira, H. Huang, D. Chen, F. Butzke, Z. Li, M. Gibiluka, M. Breuer, N. Calazans and Peter Beerel, "Blade - A Timing Violation Resilient Asynchronous Template," in *ASYNC 2015*, pp. 21–28.

▶ 44

Asynchronous Control Circuit Design - L2 5/28/2016

Resilient Bundled Data

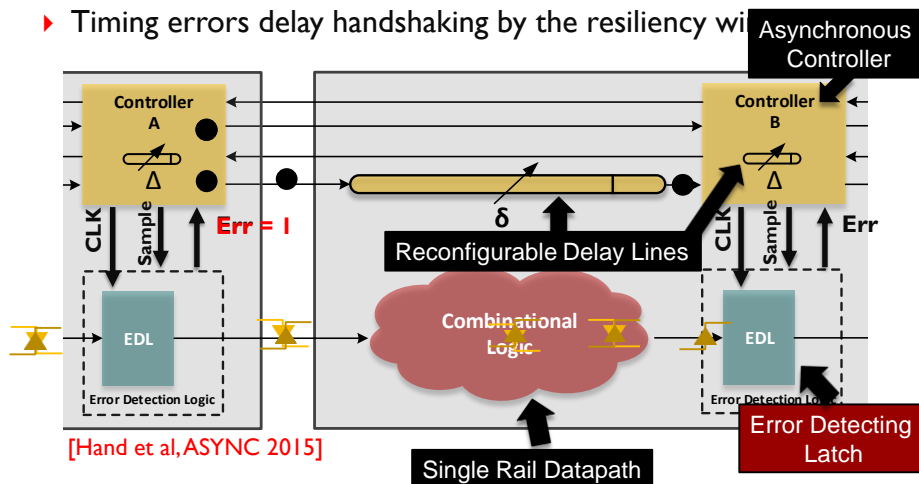- Timing errors delay handshaking by the resiliency with



► 45

Asynchronous Control Circuit Design - L2 5/28/2016

C Element Extensions and Generalizations

►

Boolean Function with Feedback

- ▶ **Define:**
 - ▶ SET, KEEP and RESET functions which are feedback free
 - ▶ $\text{RESET} = \text{U} - \text{SET}$ (OFF-set of SET), or
 - ▶ $\text{RESET} \cap \text{SET} = \emptyset$
 - ▶ $\text{KEEP} = \text{RESET}'$
 - ▶ **Sole feedback of f is on the f line** (feeds back to input)
- ▶ **Form 1 (Set and Keep):**
 - ▶ $f = (\text{SET function}) + f$ (KEEP function)
- ▶ **Form 2 (Set and Reset):**
 - ▶ $f = (\text{SET function}) + f$ (RESET function)'
- ▶ **Example**
 - ▶ Asymmetric C Element:
 - ▶ $f = bc$ (SET) + f (ab')' (RESET)'

▶ 47


Asynchronous Control Circuit Design - L2 5/28/2016

Composing C Elements

- ▶ **Based on the C-Element Boolean Equation:**
 - ▶ 2-input C-Element's Logic Function is:

$$c = ab + c(a + b) = ab + bc + ac$$
 - ▶ n-input C-Element is:

$$c = a_1 a_2 \dots a_n + c(a_1 + a_2 + \dots + a_n)$$
- ▶ **It can be shown that C gates are composable using their *set*, *keep* functions:**
 - ▶ $c3_{\text{set}} = a1a2a3$, $c3_{\text{keep}} = a1 + a2 + a3$
 - ▶ $c2_{\text{set}} = a1a2$, $c2_{\text{keep}} = a1 + a2$
 - ▶ $o_{\text{set}} = a1a2$, $o2_{\text{keep}} = a1 + a2$
 - ▶ $\text{output}_{\text{set}} = (o_{\text{set}} \cdot a3)$, $\text{output}_{\text{keep}} = (o_{\text{keep}} + a3)$
- ▶ **Thus:**
 - ▶ $o_{\text{set}} = c3_{\text{set}}$, $\text{output}_{\text{keep}} = c3_{\text{keep}}$

 


▶ 48

Asynchronous Control Circuit Design - L2 5/28/2016

Asymmetric C Elements

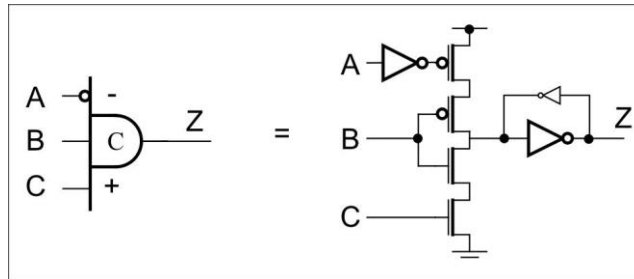- ▶ In certain cases, the Set and Reset logic of a C element is not identical
 - ▶ Obvious from PTnet specification of a controller
- ▶ Asymmetric C elements are an extension of the basic C
- ▶ Equivalent to SR Latch or Boolean feedback circuit as well




▶ 49

Asynchronous Control Circuit Design - L2 5/28/2016

Taxonomy of Latch Controllers

▶


Taxonomy of Latch Controllers - Signals

 

51

Asynchronous Control Circuit Design - L2 5/28/2016


Taxonomy of Latch Controllers - Timing

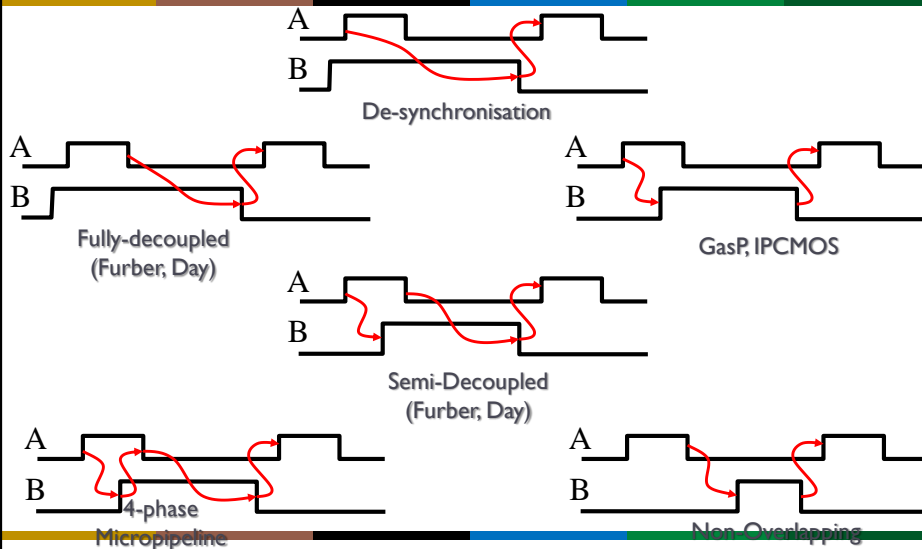


52

Asynchronous Control Circuit Design - L2 5/28/2016

Semi-Decoupled Latch Controller

 

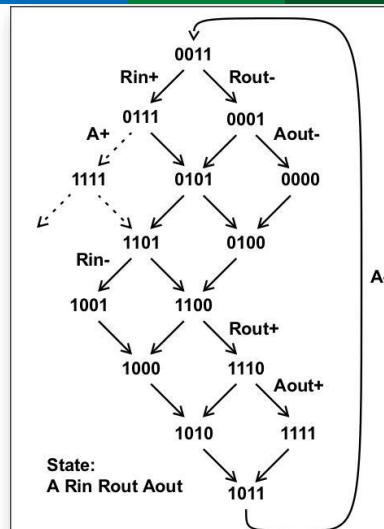
- ▶ A is redundant – ignore
 - ▶ pre-buffered Lt
- ▶ Lt is for active-low latch,



Semi-Decoupled Latch Controller PTnet

► Latch Control


- L
- L-, L+ in PTnet

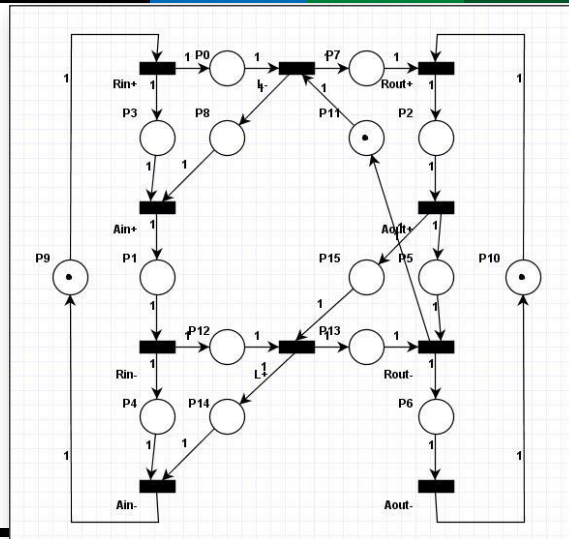

► 55

Asynchronous Control Circuit Design - L2 5/28/2016

Semi-Decoupled Latch Controller Circuit

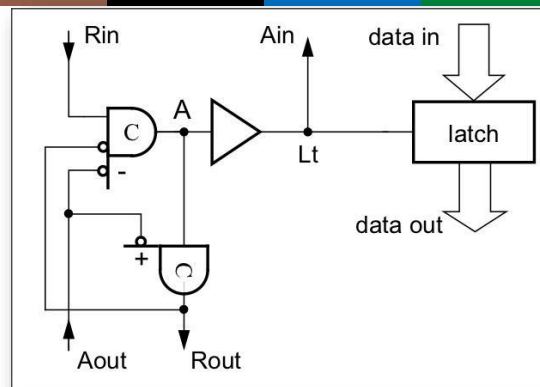


- C-gate Set, Reset functions may be inferred from STG/PTnet specification of the controller

► 56

Asynchronous Control Circuit Design - L2 5/28/2016

Semi-Decoupled – PTnet for 3 Stages

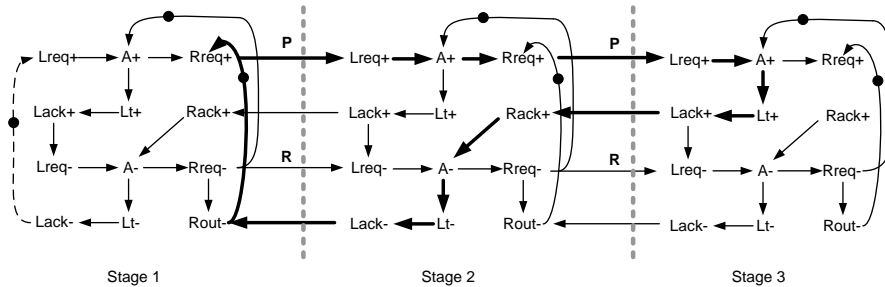

*Notice how critical cycle contains two “P”s
(i.e., processing steps involving delay lines)*


► **Is this an issue? Why?**

► 57


Asynchronous Control Circuit Design - L2 5/28/2016

Fully-Decoupled Latch Controller

 Fully-Decoupled Latch Controller – STG and SG



 - ▶ A again is redundant
- ▶ Lt is for active-low latch,
- ▶ B is internal signal
- ▶ Needed for implementation




▶ 59

Asynchronous Control Circuit Design - L2 5/28/2016

Fully-Decoupled Latch Controller PTnet

 
- ▶ Latch Control
 - ▶ L
 - ▶ L-, L+ in PTnet
- ▶ Signal INT,
 - ▶ Transitions INT+/INT-
 - ▶ Internal
 - ▶ For implementation purposes only



▶ 60

Asynchronous Control Circuit Design - L2 5/28/2016

Fully-Decoupled Latch Controller Circuit

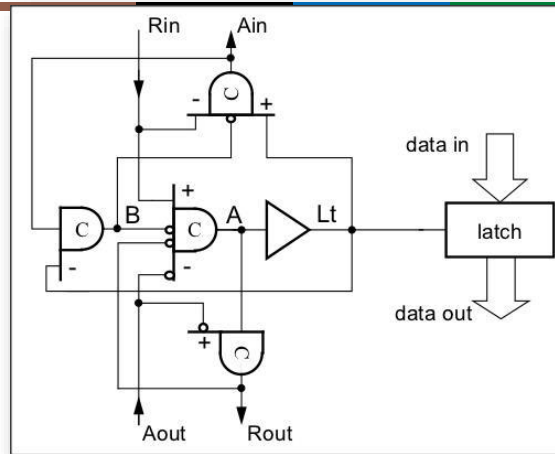

- ▶ Note Tradeoff between Concurrency and Circuit Complexity
- ▶ **PTnet concurrency is not confluent with circuit**


▶ 61

Asynchronous Control Circuit Design - L2 5/28/2016

2 C-Element De-synchronisation
Controller

▶

 2 C-Element De-Synchronisation Controller




- ▶ Master Latch Enable: $M = (Ain \neq Rout)$ [XOR gate]
- ▶ Slave Latch Enable: $S = (Rout == Aout)$ [XNOR gate]

▶ 63

Asynchronous Control Circuit Design - L2 5/28/2016

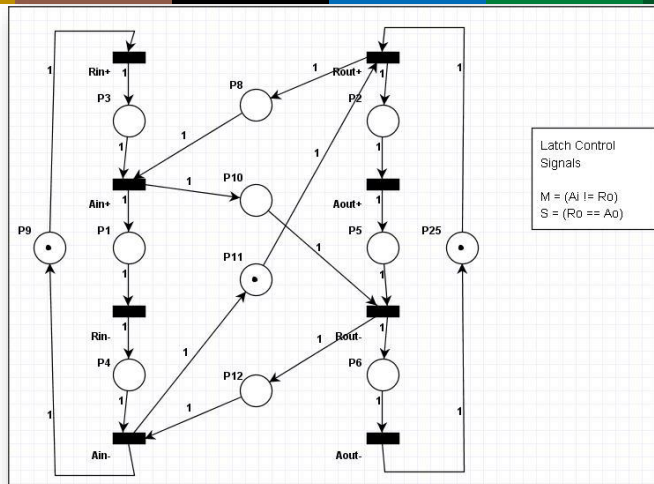2 C-Element De-Synchronisation Controller – Handshake Signals PTnet




- ▶ C elements obvious from PTnet Signal dependencies

▶ 64

Asynchronous Control Circuit Design - L2 5/28/2016

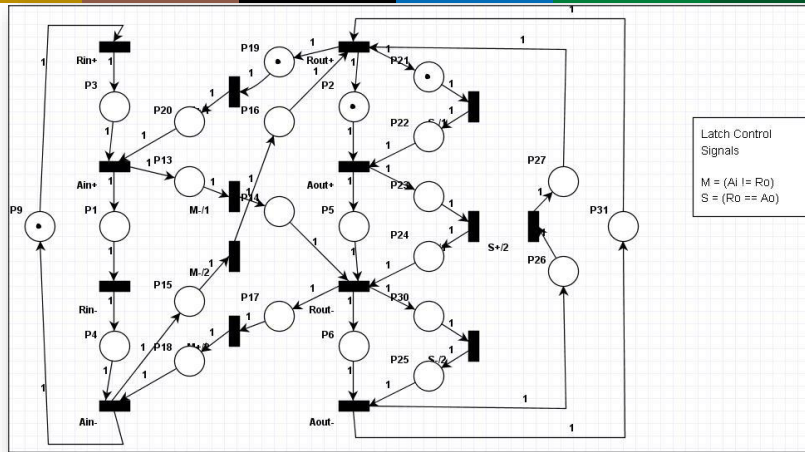2 C-Element De-Synchronisation Controller




► Need multiple instantiations of M, S signals

► Per control signal transition

► 65

Asynchronous Control Circuit Design - L2 5/28/2016

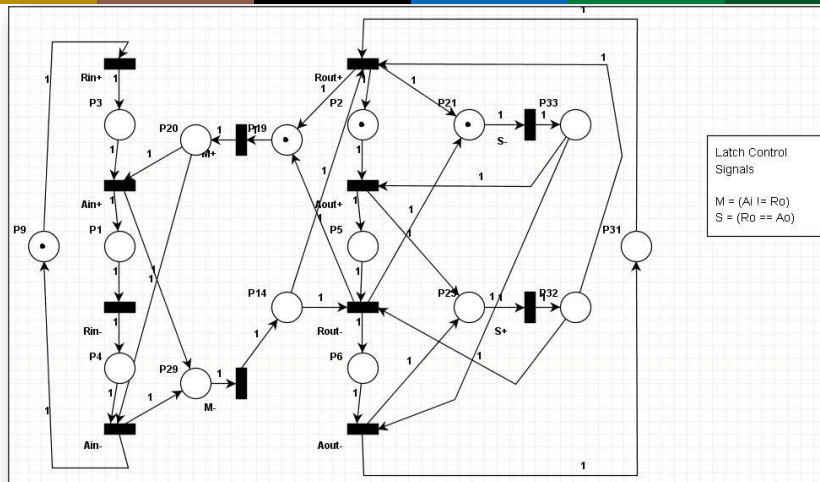2 C-Element De-Synchronisation Controller – How to Merge M, S Signals using Choice




► Note: PTnet is now AC

► 66


Asynchronous Control Circuit Design - L2 5/28/2016

2 C-Element De-Synchronisation Controller Analysis - PTnets

 ► Reduction to Latch Control Signals (Verify)



► Characteristic Pattern:

 


► 67

Asynchronous Control Circuit Design - L2 5/28/2016

De-Synchronisation Maximum
Concurrency Controller

►

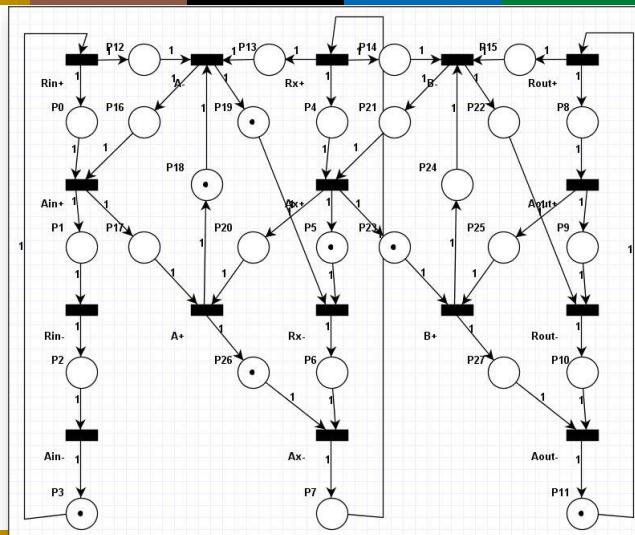De-Synchronisation Maximum Concurrency Controller



► 69

Asynchronous Control Circuit Design - L2 5/28/2016

Bundled-Data Design: Summary

- Similar area to synchronous circuit
- Enables the use of
 - standard-cell cell libraries, conventional EDA tools
- Performance improvements due to
 - **PVT variation tracking**, with post-silicon tuning of delay lines
 - Pipeline stages can achieve **average-case delay**, using
 - **multiplexed delay lines** (operand-based delay), and/or
 - **error detecting latches**
- Power benefits
 - Dynamic voltage scaling
 - Conditional communication
- Workhorse of several Asynchronous start-ups
 - Nanochronous, Elastix, and REM

► 70

Asynchronous Control Circuit Design - L2 5/28/2016