



Asynchronous Design Seminar at University of Verona – Lecture Notes 1

Asynchronous Design Fundamentals



Lecture Notes 1

- ▶ **Motivation for Asynchronous Design**
 - ▶ Challenges in Traditional Synchronous Design
 - ▶ Benefits of Asynchronous Design
 - ▶ Startup and other Industrial Efforts (Past and Current)
 - ▶ Challenges and Opportunities Moving Forward
- ▶ **Data Channels and Channel Based Design**
- ▶ **Handshaking and its impact**
- ▶ **Asynchronous Pipelines**
 - ▶ Data Token Movement and Control
 - ▶ Characteristics and Performance
- ▶ **Modelling using PTnets**
- ▶ **Latch Controller Design**

Motivation

CHALLENGES

VARIATIONS

COMPLEXITY

COST

GOALS

P

Power

P

Performance

A

Area

Everything else:
Design cost,
complexity, risk,
time-to-market

MEANS

NOC

SOC

REUSE

Sub-VT
Near-VT


Neuro-
morphic

► 3

Asynchronous Control Circuit Design - LI 5/25/2016

Motivation I: Network on Chip

 - Scale of chip / designs increasing
- Design efficiency demands network on chip
- Synchronous NoCs challenging
 - Span large portion of chips
 - Hard to clock gate
 - Synchronization penalties
 - Impacted severely by global PVT variations
 - Buffering to reduce contention is costly




Tiler's TILE-Mx100

► 4

Asynchronous Control Circuit Design - LI 5/25/2016

Motivation II: Dynamic Variations

 


[De, Asian IIEEE ASSCC 2014]

- Dynamic variations force margins on clock frequency

► 5


Asynchronous Control Circuit Design - LI 5/25/2016

Motivation III: Near Threshold Computing

 

[Borkar, et al. DAC 2012]

 - NTV computing provides ~5X energy efficiency
- But margins grow by ~5x forcing constrained libraries and flows




[Dreslinksi et al., IEEE Proc. 2010]

► 6

Asynchronous Control Circuit Design - LI 5/25/2016

Motivation IV: Neuromorphic Computing

 

- ▶ Neuromorphic cores
- ▶ Large scale
 - ▶ hard to route a global clock everywhere
- ▶ Low activity
- ▶ Asynchronous becoming default approach




▶ 7

Asynchronous Control Circuit Design - LI 5/25/2016

Motivation V: Metastability

 
- ▶ Multiple clock domains, and dynamic frequency scaling
- ▶ Crossings are hard, challenging, risky
- ▶ Subject to variations and modes of use
- ▶ Understanding comes from theory of asynchronous circuits
- ▶ Solutions
 - ▶ Synchronizer design and verification
 - ▶ Arbiters
 - ▶ Encapsulate the issues



▶ 8

Asynchronous Control Circuit Design - LI 5/25/2016

The Asynchronous Alternative

 


Synchronization and communication between blocks implemented with asynchronous channels that send and receive tokens

► 9

Asynchronous Control Circuit Design - LI 5/25/2016

Concurrent Communicating Hardware

 
- System is a collection of **Processes** linked by **Channels**
- Channels pass messages with **guaranteed delivery**
- Processes synchronize
- Processes can be **decomposed** into smaller processes




► 10

Asynchronous Control Circuit Design - LI 5/25/2016



Asynchronous Channels

 

Bundled-Data Channel

 

Dual-Rail (1-of-N) Channel

 
 


1 of the N wires rises
(N-1 remains zero)

► 11

Asynchronous Control Circuit Design - LI 5/25/2016

Asynchronous Blocks

  

► Bundled-Data

- Delay line Matched to Worst-Case Combinational Logic Delay
- May be Post-silicon Tunable
- Uses Standard-Cell Libraries

► QDI

- Data and Completion integrated
- Relies on Completion Sensing Logic
- Uses Proprietary Cell Libraries
 - Domino-Style Dynamic Logic

► 12

Asynchronous Control Circuit Design - LI 5/25/2016

Performance Advantages

- ▶ **Freedom from global clock(s)**
 - ▶ Local versus global control supports higher frequencies with less effort
 - ▶ Flexible pipelining – block- to gate-level
 - ▶ Efficient Support for Globally Asynchronous Locally Synchronous (GALS) Design
- ▶ **Average-case delay**
 - ▶ Architectural – Optimize Architecture for the Common Data Flow
 - ▶ Micro-architectural – Optimize Blocks for Average-case Input Data
 - ▶ Gate-level – Control Responds to Average Delays (e.g. Metastability)
 - ▶ Process – Design Adapts to Process Variation (e.g. Tunable Delay Lines)
 - ▶ Voltage – Design Adapts to Voltage (e.g. Dynamic Voltage Scaling)
 - ▶ Temperature – Design Adapts to Temperature (e.g. Wide Temperature range)
 - ▶ Also leads to Power Advantages!

▶ 13

Asynchronous Control Circuit Design - LI 5/25/2016

Power Advantages

- ▶ **Automatically adapts to operating conditions and variations**
 - ▶ Combines: voltage/frequency scaling, clock-gating, tuning
 - ▶ More power savings, than the sum of all these techniques
- ▶ **Clock-gating inherent in most asynchronous designs**
 - ▶ Only expend energy in blocks when blocks are used
 - ▶ Inherent in architectural level rather than as an after-thought
- ▶ **Blocks can be designed at ideal throughput**
 - ▶ Rather than dictated by global clock period
 - ▶ Less frequently used blocks can be designed at lower throughput
- ▶ **Immediate start-up (no need to wait for clock to stabilize)**
 - ▶ Go quiet; Run fast; Go quiet again

▶ 14

Asynchronous Control Circuit Design - LI 5/25/2016

Other Advantages

- ▶ **Reduced Electromagnetic Noise**
 - ▶ No global clock
 - ▶ Frequency spread out much more
 - ▶ Co-locate with sensitive analog
 - ▶ Less noise - does not effect analog circuitry
- ▶ **Ease of Modular Composition**
 - ▶ Reduces design complexity, cost, risk, iterations, time to market
 - ▶ Supports GALS design for multi-frequency disparate SoC designs
 - ▶ Handshaking offers plug-and-play IP

▶ 15

Asynchronous Control Circuit Design - LI 5/25/2016

Asynchronous Challenges (1 of 2)

- ▶ **CAD tools**
 - ▶ Support from major EDA companies
- ▶ **Cell/IP Core Libraries for Asynchronous Design**
 - ▶ Most design styles could benefit from at least a few asynchronous cells
 - ▶ e.g., C-elements, Mutual Exclusion Elements
 - ▶ Some design styles heavily rely on custom gates
 - ▶ QDI PCHB, NCL
- ▶ **High-performance asynchronous design**
 - ▶ Some blocks can be 2-5x larger due to dual-rail design
 - ▶ May consume more peak power than desired
- ▶ **Low-power asynchronous design**
 - ▶ Can be slower than desired, if control overhead not managed

▶ 16

Asynchronous Control Circuit Design - LI 5/25/2016

Asynchronous Challenges (2 of 2)

- ▶ **Debug**
 - ▶ Circuit can't be slowed via clock to aid in debugging
 - ▶ ...but the circuit can be single-stepped more easily!

- ▶ **Asynchronous test**
 - ▶ Testers geared toward synchronous
 - ▶ Standards do not exist and test methodologies still evolving
 - ▶ Automatic test pattern generation in infancy

▶ 17

Asynchronous Control Circuit Design - LI 5/25/2016

Asynchronous Commercialization Efforts (1 of 2)

- ▶ **Fulcrum Microsystems** (www.fulcrummicro.com)
 - ▶ High-performance computing and networking markets
 - ▶ Founded out of Caltech in 2000, Sold to Intel in 2011
 - ▶ Several asynchronous products shipping, Full-custom flow still in use today
- ▶ **TimeLess Design Automation**
 - ▶ High-Performance ASIC Flow for Asynchronous Design
 - ▶ Founded out of USC in 2008
 - ▶ Sold to Fulcrum Microsystems in 2010
 - ▶ Semi-custom flow still in use today
- ▶ **Achronix** (www.achronix.com)
 - ▶ High-performance async FPGA core with synchronous interfaces
 - ▶ Founded out of Cornell research in 2006
 - ▶ Speedster®22i HP is shipping and includes fine-grain asynchronous pipelines

▶ 18

Asynchronous Control Circuit Design - LI 5/25/2016

Asynchronous Commercialization Efforts (2 of 2)

- ▶ **Tiempo** (www.tiempo-ic.com)
 - ▶ IP Cores and ASIC Flow (Power/Performance Tradeoff)
 - ▶ Smartcards ...
- ▶ **vSync Circuits** (www.vsyncc.com)
 - ▶ EDA and IP for Multi-Clock Domain design integration and verification
- ▶ **Reduced Energy Microsystems** (remicro.systems)
 - ▶ Low Power ASIC microprocessors using asynchronous resiliency
 - ▶ Founded in 2015 – Newest kid on the block
- ▶ **IBM**
 - ▶ Neuromorphic True North core based on QDI technology (EXPAND)
- ▶ **Several Past Start-ups**
 - ▶ Handshake Solutions,
 - ▶ Silistix,
 - ▶ Elastix, Nanochronous,
 - ▶ Cogency


Channel-Based Design

Top-Level View of Asynchronous Circuits

Hardware Abstraction

► System:

 - Collection of “**Processes**” linked by **Channels**
- Channels pass messages with **guaranteed delivery**
- Processes synchronize
- Processes can be **decomposed** into smaller processes




► 21

Asynchronous Control Circuit Design - LI 5/25/2016

Synchronous Version

► In case of edge triggered stages

 - During the cycle: Process
- At the edge of the clock: Pass to successor




► 22

Asynchronous Control Circuit Design - LI 5/25/2016

Synchronous Version

► Central synchronizer

► `SYNC(clk)

 

```
module ff(clk, left, right)
input      clk;
input      left;
output reg right;

always
begin
`SYNC(clk);
right = left;
end
endmodule
```

Synchronous FF Stage

► Abstract synchronization

► `SYNC(clk)

```
module ff(clk, left, right)
input      clk;
input      left;
output reg right;

always @(posedge clk) begin
right = left;
end
endmodule
```

```
module ff(clk, left, right)
input      clk;
input      left;
output reg right;

always
begin
`SYNC(clk);
right = left;
end
endmodule
```

Asynchronous Version

► Distributed Synchronization

► Sender

- Provides data
- Synchronize

► Receiver


- Synchronize
- Samples data

```
module Sender(right)
output reg    right;
output reg    data;

always
begin
right = data;
`SYNC(right);
end
endmodule
```

```
module Receiver(left)
input         left;
output reg    data;

 always
begin
`SYNC(left);
data= left;
end
endmodule
```




► 25

Asynchronous Control Circuit Design - LI 5/25/2016

Asynchronous Channels

► **Channel:** A bundle of wires and a protocol for communicating data/control called a **token**

 
- **Data/control encoding:** Dual-rail or Single-rail encoded
 - tells what the data is, and when it is valid
- **Communication protocol:** Handshake over request/acknowledgement wires





► 26

Asynchronous Control Circuit Design - LI 5/25/2016


Asynchronous Channel Types

 

Bundled-Data Channel

  

Dual-Rail (1-of-N) Channel

 


1 of the N wires is risen
(N-1 remains zero)



► 27

Asynchronous Control Circuit Design - LI 5/25/2016


Asynchronous Channel Types

 

Bundled-Data Channel

  



Dual-Rail (1-of-2) Channel

 

1 of the 2 wires rises

► 28

  Asynchronous Control Circuit Design - LI 5/25/2016




Logic Hazards (Glitches)

▶ Synchronous Circuits

- ▶ Glitches tolerated because outputs sampled only after signals settle
- ▶ Clocking constraints
 - ▶ Clock edge occurs only after data settles
 - ▶ Limits clock frequency

▶ Asynchronous Circuits

 - ▶ Control circuits
 - ▶ Avoided completely
 - ▶ Hazard-free logic synthesis techniques
- ▶ Datapath (Either)
 - ▶ Outputs sampled after signal settles OR
 - ▶ Avoided completely



▶ 31

Asynchronous Control Circuit Design - LI 5/25/2016

Asynchronous Circuits - Classes

▶ Timing Model (or Class) is used to define specific timing assumptions with respect to correct circuit operation

▶ DI

- ▶ Arbitrary gate and wire delays (unbounded)

▶ QDI


- ▶ DI except for Isochronic Forks
 - No need to acknowledge fanouts

▶ SI (Muller) circuits

- ▶ Arbitrary gate delay no wire delay
- ▶ Only applicable to small-scale control circuits

▶ Fundamental Mode (Huffman) circuits

 
- ▶ Outputs and Local State (internal) stabilize
 - before a new input change from the circuit's environment



▶ 32

Asynchronous Control Circuit Design - LI 5/25/2016

2-Phase Bundled-Data



 


- ▶ **Two-phase Bundled-Data Protocol**
 - ▶ Both rising and falling transitions on Req
 - ▶ Means new data are available
- ▶ **Both rising and falling transitions on Ack**
 - ▶ Means data have been acknowledged
- ▶ **Sometimes called transition signaling**
 - ▶ It is the transition that is meaningful (stateful), not the level values
- ▶ **Push Channels**
 - ▶ Pull Channels shortly

▶ 33

Asynchronous Control Circuit Design - LI 5/25/2016

1-of-N Protocols

  
 


- ▶ **Dual-Rail**
 - ▶ 4 phase
 - ▶ 2 wires per bit
- ▶ **1-of-4**
 - ▶ 4 phase
 - ▶ 4 wires per 2 bits

▶ 34


Asynchronous Control Circuit Design - LI 5/25/2016

Pull Channels

  


▶ Early:

 - ▶ Data stable after Ack+
- ▶ Data stable until Req-



▶ Late:

 - ▶ Data stable after Ack-
- ▶ Data stable until Req+




▶ Broad:

- ▶ Data stable after Ack+
- ▶ Data stable until Req-


▶ 35

Asynchronous Control Circuit Design - LI 5/25/2016


Abstract Channel Diagrams

 

▶ Push Channel

 

▶ Pull Channel

 

- ▶ Synchronization channel – no data attached/bundled
 - ▶ No data – Control only
 - ▶ Active on right side

Handshaking details omitted


▶ 36

Asynchronous Control Circuit Design - LI 5/25/2016

Sequencing and Concurrency

▶ Enclosed Handshaking

 - ▶ B completes handshake with C before starting handshake with D
 - ▶ Operation associated with C occurs before operation associated with D
- ▶ B can enclose both handshakes in handshake with A
 - ▶ Completion of handshake with A is acknowledgement that the tasks of C and D are done



▶ Pipelining Handshake

- ▶ B overlaps handshake with C and handshake with A
- ▶ Creates pipeline behavior
 - ▶ Tokens flow on both channels
- ▶ Increases throughput



▶ 37

Asynchronous Control Circuit Design - LI 5/25/2016


Token Buffer Pipelines

Pipelining Data Tokens

▶ 38

Asynchronous Control Circuit Design - LI 5/25/2016

Pipelined Handshaking

 


- ▶ Pipeline handshaking enables multiple tokens to exist in pipeline
 - ▶ Each token represents intermediate result of different problem instance
 - ▶ Increases throughput of system
- ▶ No tokens lost despite relative speed of stages – has implicit flow control
- ▶ Two types
 - ▶ Full buffers can support distinct tokens on inputs/output channels
 - ▶ Half buffers cannot support distinct tokens on inputs/outputs
 - ▶ N-stage pipeline of half-buffers can support a maximum of $N/2$ tokens

▶ 39

Asynchronous Control Circuit Design - LI 5/25/2016

Full-Buffer Handshaking

 - ▶ Pipeline can store tokens at every buffer




Handshaking assuming Bit Bucket is Stalled

▶ 40

Asynchronous Control Circuit Design - LI 5/25/2016

Half-Buffer Handshaking

 


▶ Constraint that leads to a half-buffer:

- ▶ output channel must be acknowledged before input channel completes handshake

▶ e.g., $c1ack+$
before $c0ack-$

▶ Pipeline can store tokens at every other buffer

 
Handshaking assuming Bit Bucket is Stalled



▶ 41

Asynchronous Control Circuit Design - LI 5/25/2016

Conditional and Non-Linear Pipeines

 

▶ MERGE

- ▶ Wait for token on S.
- ▶ Depending on value, wait for token on either A or B and send onto O


▶ SPLIT

- ▶ Wait for token on S and A.
- ▶ Dependent upon value of S, send copy of token on A to O1 or O2

▶ 42

Asynchronous Control Circuit Design - LI 5/25/2016

Timing Diagram of Merge

 

Assumptions (in this example)

- Full-buffer Two-phase Handshaking
- dual-rail select signal


Functionality – Handshake MUX

- Token on A consumed first
 - After token on $S = 0$
 - i.e., $S0$ changes
- Token on B stalled until consumed second
 - After token on $S = 1$
 - i.e., Once $S1$ changes
- Result: two tokens on O
 - First = $Oreq+$
 - Second = $Oreq-$

► 43

Asynchronous Control Circuit Design - LI 5/25/2016

Send and Receive Cells

 

SEND

- Always receive on L and E.
- Conditionally send on R if $E == 1$.

RECV

- Always receive on E and send on R.
- Conditionally receive on L if $E == 1$.

► 44

Asynchronous Control Circuit Design - LI 5/25/2016

Asynchronous Pipelines

Dynamic behavior is very different from synchronous design

► 45



Asynchronous Control Circuit Design - LI 5/25/2016

Synchronous vs. Asynchronous Pipelines

► Intuitive Understanding of the Differences

► 46

  Asynchronous Control Circuit Design - LI 5/25/2016




Synchronous vs. Asynchronous

- ▶ Tokens represent Data
 - ▶ Data Tokens
- ▶ We now compare the Synchronous and Asynchronous Data Flows in the simplest version of this datapath
- ▶ Synchronous version first...

▶ 49



Asynchronous Control Circuit Design - LI 5/25/2016



Synchronous Token Movement


 




▶ 50

  
Asynchronous Control Circuit Design - LI 5/25/2016



  

 
 


 
 



 


Synchronous Token Movement

  - ▶ Tokens are always separated by empty latches
 - ▶ Aka “Bubbles”
- ▶ Latency is strongly dependent on # of clock cycles
- ▶ Pipeline delays result in cycle-based Latency increase
- ▶ Now, let’s look at the Asynchronous version...



  

  

Asynchronous Token Movement

- ▶ Latency depends on combinational cloud delays
 - ▶ Not multiple of a clock, data-dependent
- ▶ Token Speed depends on available space in pipeline stages
 - ▶ Contention reduces performance!
 - ▶ Similarly to people in a queue (line)
 - ▶ Increasing pipe stages can:
 - ▶ Increase Tokens/sec, i.e. Performance
 - ▶ Reduce Latency, if Local Delays are Improved,
 - e.g. wire buffering
- ▶ Notion of total (or max/min) Tokens in the system, and total (or max/min) empty token buffers (bubbles)
 - ▶ System-Level optimization issue

▶ 73

Asynchronous Control Circuit Design - LI 5/25/2016

Petri Nets (PN) in a Nutshell

- ▶ A PN is a graph of **Places** and **Transitions**
 - ▶ Allowed connections
 - ▶ Places are connected to Transitions
 - ▶ Transitions are connected to Places
- ▶ **Places**
 - ▶ Places hold a token (in general can be more than 1)
 - ▶ A place with a token is active (marked)
- ▶ **Transitions**
 - ▶ A transition is activated (fires)
 - ▶ when tokens are available on all of its input places
 - ▶ When it fires
 - ▶ it creates new tokens on all of its output places
- ▶ PN can model both
 - ▶ Choice, Return from Choice
 - ▶ Fork and Join


▶ 74

Asynchronous Control Circuit Design - LI 5/25/2016

High-Level Asynchronous Pipeline: PTnet Models

► Full Buffer High-Level Model

 - Used to analyze and optimize Throughput and Latency:




► 75

Asynchronous Control Circuit Design - LI 5/25/2016

High-Level Asynchronous Pipeline PTnet Models

► Full Buffer and Half Buffer High-Level Models

 - Used to analyze and optimize Throughput and Latency:



► 76

Asynchronous Control Circuit Design - LI 5/25/2016

Dynamic Pipeline Behavior

- ▶ Cycle Time
 - ▶ $T = FL + BL$ (simplest case)
- ▶ Latency
 - ▶ input to output delay = $N * FL$
- ▶ Throughput
 - ▶ # of tokens flowing per unit time, generally = $I/T = I/(FL + BL)$
 - ▶ Depends on throughput of sender/receiver
- ▶ Static Slack or Static Token Occupancy
 - ▶ Maximum token capacity of the pipeline
- ▶ Spread
 - ▶ distance between successive tokens in an optimally-filled pipeline
 - ▶ token distance travelled for $I T = (FL + BL)/I$
- ▶ Dynamic Slack or Dynamic Occupancy
 - ▶ Average token capacity in the pipeline at optimal throughput
 - ▶ $N * I / \text{Spread} = (N * FL) / (FL + BL)$

▶ 77

Asynchronous Control Circuit Design - LI 5/25/2016


Dynamic Pipeline Behavior

- ▶ Cycle Time
 - ▶ $T = FL + BL$ (simplest case)
- ▶ Latency
 - ▶ input to output delay = $N * FL$
- ▶ Throughput
 - ▶ # of tokens flowing per unit time, generally = $I/T = I/(FL + BL)$
 - ▶ Depends on throughput of sender/receiver
- ▶ Static Slack or Static Token Occupancy
 - ▶ Maximum token capacity of the pipeline
- ▶ Dynamic Slack or Dynamic Occupancy
 - ▶ Average token capacity in the pipeline at optimal throughput
 - ▶ $N * I / \text{Spread} = (N * FL) / (FL + BL)$

▶ 78

Asynchronous Control Circuit Design - LI 5/25/2016

Dynamic Occupancy, Throughput

 


- Dynamic Slack or Dynamic Occupancy
Formula for N buffers:

$$\frac{N * FL}{FL + BL} = \frac{N}{1 + \frac{BL}{FL}}$$

- Assumptions:

 
- Tokens not stalled by buffers or Bit Bucket resetting
- Tokens inserted at rate of local cycle time (FL + BL)
- Tokens consumed at rate of local cycle time



► 79

Asynchronous Control Circuit Design - LI 5/25/2016

Throughput vs. Tokens Graph

 


- Throughput is zero

- When no tokens in pipe
- When pipeline is full of tokens

- Peak throughput in-between

 - Token limited region
 - Faster Bit Gen improves throughput
- Bubble limited region
 - Faster Bit Bucket improves performance



► 80


Asynchronous Control Circuit Design - LI 5/25/2016

Example: Pipeline Performance

► Slow left environment

- Bit Gen: LCT = 6
- Buffer: FL=2, BL=2
- Bit Bucket: LCT = 2

 $t=0$: Token 1 generated
 $t=6$: Token 2 generated
 $t=12$: Token 3 generated
 $t=18$: Token 4 generated
 $t=24$: Token 5 generated



► 81


Asynchronous Control Circuit Design - LI 5/25/2016

Example: Pipeline Performance

► Slow right environment

- Bit Gen: LCT = 2
- Buffer: FL=2, BL=2
- Bit Bucket: LCT = 6


 
$t=6$: Token 1 consumed
 $t=12$: Token 2 consumed
 $t=18$: Token 3 consumed
 $t=24$: Token 4 consumed



► 82

Asynchronous Control Circuit Design - LI 5/25/2016

Concrete Example: 3-stage Pipeline

  


83

Asynchronous Control Circuit Design - LI 5/25/2016

More Complex Example: Pipeline Performance

- What is the impact of fork/join on asynchronous pipelines?
- Assume FL = 1, BL = 1

4, 3 Fork Join

 

84


Asynchronous Control Circuit Design - LI 5/25/2016

More Complex Example: Pipeline Performance

- What is the impact of fork/join on asynchronous pipelines?

Assume $FL = 1, BL = 1$

4, 2 Fork Join

 

85


Asynchronous Control Circuit Design - LI 5/25/2016

More Complex Example: Pipeline Performance

- What is the impact of fork/join on asynchronous pipelines?

Assume $FL = 1, BL = 1$


4, 1 Fork Join

 

86

Asynchronous Control Circuit Design - LI 5/25/2016

Key to High Performance – Slack Matching

 

► The Slack Matching Problem:

- Add minimum number of pipeline buffers to the circuit to meet a target T
- This problem is unique to Asynchronous Design
 - Unfortunately, often yields significant Area and Power Overhead!

► 87

Asynchronous Control Circuit Design - LI 5/25/2016


Latch Control Circuits

Basic Example of Latch Control

► 88

Asynchronous Control Circuit Design - LI 5/25/2016

 
Bundled-Data Control Circuits – Basic Latch Control



▶ 89

Asynchronous Control Circuit Design - LI 5/25/2016


C Gate – PN to STG Conversion

 

▶ 90

Asynchronous Control Circuit Design - LI 5/25/2016

 
Condition 1: Latch Should Not Open until Successor Latch has Captured Data



► 91

Asynchronous Control Circuit Design - LI 5/25/2016

 Condition 1: Latch Should Not Open until Successor Latch has Captured Data




► 92

Asynchronous Control Circuit Design - LI 5/25/2016

Asynchronous Control Circuit Design - LI 5/25/2016

Asynchronous Control Circuit Design - LI 5/25/2016

 
Latch Control Signal Dependencies Imposed by Condition 1



► 95

Asynchronous Control Circuit Design - LI 5/25/2016

 
Latch Control Signal Dependencies Imposed by Condition 1



► 96

Asynchronous Control Circuit Design - LI 5/25/2016

 
Latch Control Signal Dependencies Imposed by Condition 1



► 97

Asynchronous Control Circuit Design - LI 5/25/2016

 
Condition 2: Latch Should Not Close until Captured Data from Predecessor



► 98

Asynchronous Control Circuit Design - LI 5/25/2016

 
Condition 2: Latch Should Not Close until Captured Data from Predecessor



99

Asynchronous Control Circuit Design - LI 5/25/2016

 
Condition 2: Latch Should Not Close until Captured Data from Predecessor



100

Asynchronous Control Circuit Design - LI 5/25/2016

 
Condition 2: Latch Should Not Close until Captured Data from Predecessor



► 101

Asynchronous Control Circuit Design - LI 5/25/2016

 
Latch Control Signal Dependencies Imposed by Conditions 1 and 2



► 102

Asynchronous Control Circuit Design - LI 5/25/2016

 Folded Latch Control Signal Dependencies Imposed by Conditions 1 and 2



▶ 103

Asynchronous Control Circuit Design - LI 5/25/2016

Formal Models For Asynchronous Control Circuit Design

- ▶ The graph model examples are really simplified **PN**
 - ▶ PN is Place, Transition Net (invented by Petri)
 - ▶ Represent Dependencies between signal transitions
 - ▶ Causality
 - ▶ Can Represent Choice
 - ▶ Multiple Signals (Places really) are active at one time
 - ▶ Represent Concurrency
- ▶ A PN is really a set of Multiple, Interacting FSMs all integrated and hidden within a single Graph!
 - ▶ Compact and Convenient
 - ▶ Ideal for Static Verification

▶ 104

Asynchronous Control Circuit Design - LI 5/25/2016